

Lecture 24


Time Domain Analysis of Transmission Lines

In this lecture you will learn:

- Time domain analysis of transmission lines
- Transients in transmission lines

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Time Domain Analysis - Basics

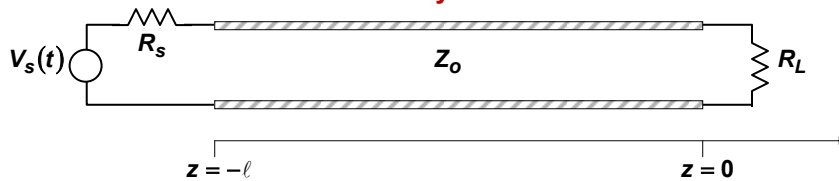

Question: How does one handle transmission lines for signals that are NOT time harmonic and when one is NOT dealing with the sinusoidal steady state?

- First thing to realize is that the notion of complex impedance has meaning only for the sinusoidal steady state
- For an arbitrary source voltage $V_s(t)$, one needs to work in the time domain and start from the basic time-domain equations:

$$\left. \begin{aligned} \frac{\partial V(z,t)}{\partial z} &= -L \frac{\partial I(z,t)}{\partial t} \\ \frac{\partial I(z,t)}{\partial z} &= -C \frac{\partial V(z,t)}{\partial t} \end{aligned} \right\} \longrightarrow \begin{aligned} \frac{\partial^2 V(z,t)}{\partial z^2} &= \frac{1}{v^2} \frac{\partial^2 V(z,t)}{\partial t^2} \\ \frac{\partial^2 I(z,t)}{\partial z^2} &= \frac{1}{v^2} \frac{\partial^2 I(z,t)}{\partial t^2} \end{aligned}$$

$$v = \frac{1}{\sqrt{LC}}$$

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Time Domain Analysis - Basics


$$Z_o$$

The equation: $\frac{\partial^2 V(z,t)}{\partial z^2} = \frac{1}{v^2} \frac{\partial^2 V(z,t)}{\partial t^2}$ $v = \frac{1}{\sqrt{LC}}$

Has forward moving solutions of the form: $V(z,t) = V_+(z - vt)$


And backward moving solutions of the form: $V(z,t) = V_-(z + vt)$

Examples:

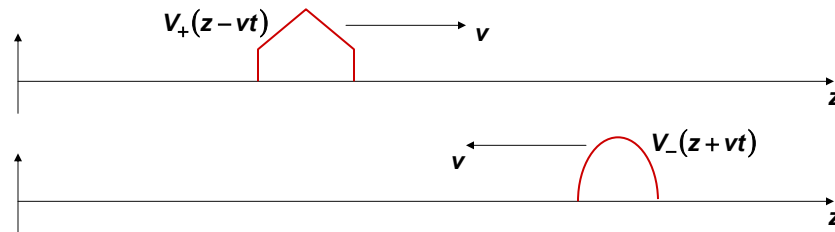

ECE 303 – Fall 2007 – Farhan Rana – Cornell University


Voltages and Currents

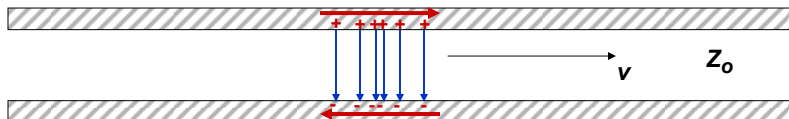

The current is related to the voltage and satisfies: $\frac{\partial V(z,t)}{\partial z} = -L \frac{\partial I(z,t)}{\partial t}$

And this: $\frac{\partial I(z,t)}{\partial z} = -C \frac{\partial V(z,t)}{\partial t}$

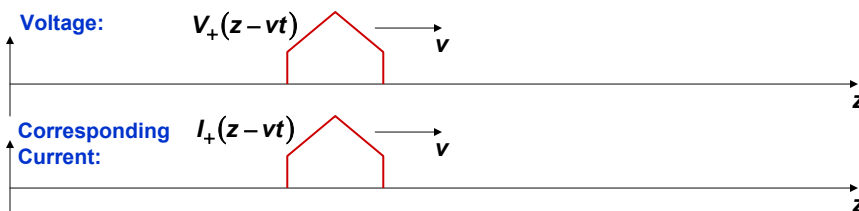
The solution is: $I_+(z - vt) = \frac{V_+(z - vt)}{Z_o}$ and $I_-(z + vt) = -\frac{V_-(z + vt)}{Z_o}$



Current is proportional to voltage since higher voltage means more surface charges and more surface charges mean more current flow

ECE 303 – Fall 2007 – Farhan Rana – Cornell University


Visualizing Propagation

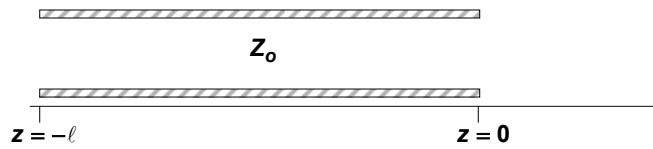


Forward moving solutions are of the form: $V_+(z - vt)$

And backward moving solutions are of the form: $V_-(z + vt)$

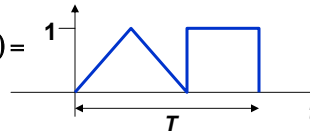So suppose somebody tells you that at $z = -\ell$: $V_+(-\ell, t) =$




Then what is the forward moving voltage on the line at $t = \ell / 2v$?

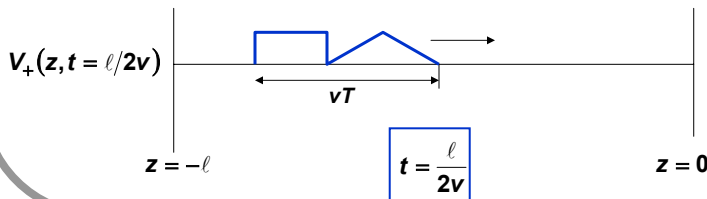

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Load End Boundary Condition

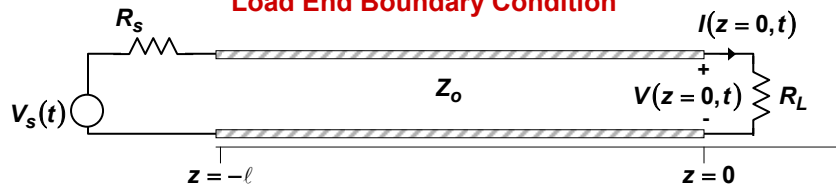

Load end boundary condition:

For all time t we must have:

$$V(z = 0, t) = I(z = 0, t)R_L$$


$$\begin{aligned} V(z = 0, t) &= V_+(z = 0, t) + V_-(z = 0, t) \\ I(z = 0, t) &= I_+(z = 0, t) + I_-(z = 0, t) \\ &= \frac{V_+(z = 0, t)}{Z_0} - \frac{V_-(z = 0, t)}{Z_0} \end{aligned}$$

Substitute these in this to get:

$$\Rightarrow V_-(z = 0, t) = V_+(z = 0, t)\Gamma_L \quad \rightarrow \quad \Gamma_L = \frac{R_L/Z_0 - 1}{R_L/Z_0 + 1}$$

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Source End Boundary Condition

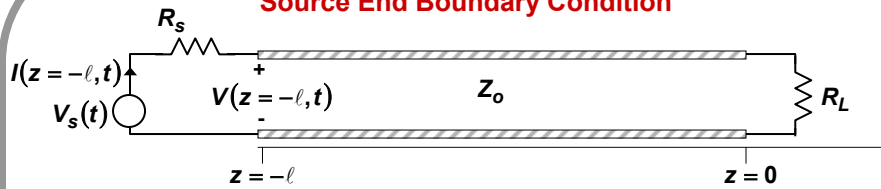

Source end boundary condition:

For all time t we must have:

$$V_s(t) = I(z = -l, t)R_s + V(z = -l, t)$$


$$\begin{cases} V(z = -l, t) = V_+(z = -l, t) + V_-(z = -l, t) \\ I(z = -l, t) = I_+(z = -l, t) + I_-(z = -l, t) \\ \quad = \frac{V_+(z = -l, t)}{Z_o} - \frac{V_-(z = -l, t)}{Z_o} \end{cases}$$

Substitute these in this to get:

$$\Rightarrow V_+(z = -l, t) = V_-(z = -l, t)\Gamma_s + V_s(t)\frac{Z_o}{R_s + Z_o} \rightarrow \left\{ \Gamma_s = \frac{R_s/Z_o - 1}{R_s/Z_o + 1} \right.$$


ECE 303 - Fall 2007 - Farhan Rana - Cornell University

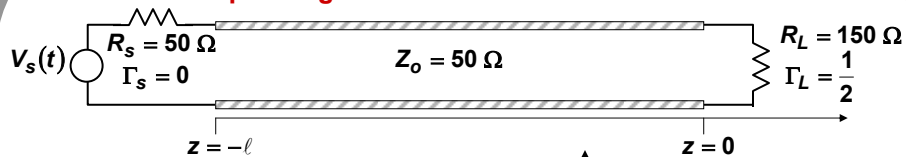Step Voltage Source: Turn-On Transient - I




Suppose the source voltage is a step function:

$$V_s(t) = 4u(t)$$

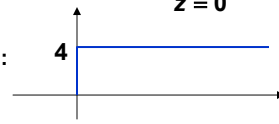


$$V_+(z = -l, t) = V_-(z = -l, t)\Gamma_s + V_s(t)\frac{Z_o}{R_s + Z_o}$$

$$\Rightarrow V_+(z = -l, t > 0) = 2$$

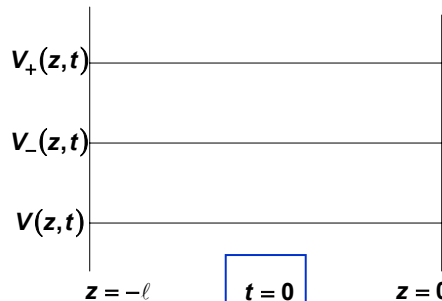



ECE 303 - Fall 2007 - Farhan Rana - Cornell University

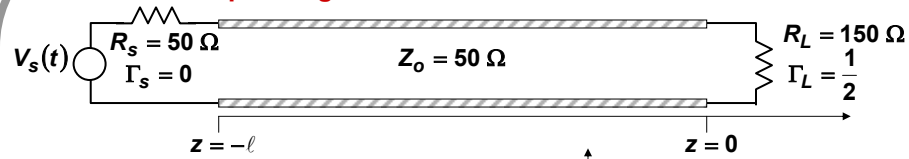Step Voltage Source: Turn-On Transient - II




Suppose the source voltage is a step function:

$$V_s(t) = 4u(t)$$

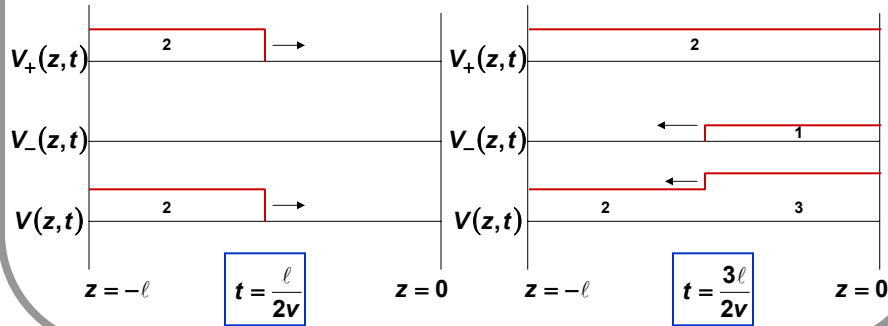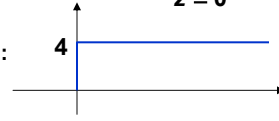


ECE 303 - Fall 2007 - Farhan Rana - Cornell University

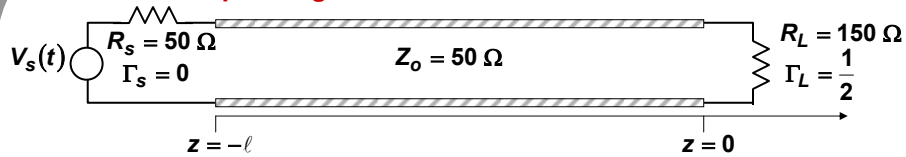Step Voltage Source: Turn-On Transient - III



- The wave reflected back from the load end does not suffer a reflection at the source end since the source impedance is matched to the line impedance

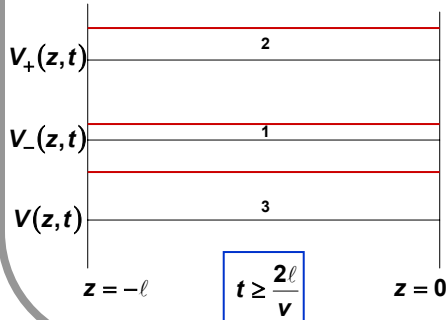
- After a time greater than $2l/v$ the line voltage is at constant 3 Volts



$$V_+(z = -l, t) = V_-(z = -l, t)\Gamma_s + V_s(t)\frac{Z_o}{R_s + Z_o}$$



ECE 303 - Fall 2007 - Farhan Rana - Cornell University

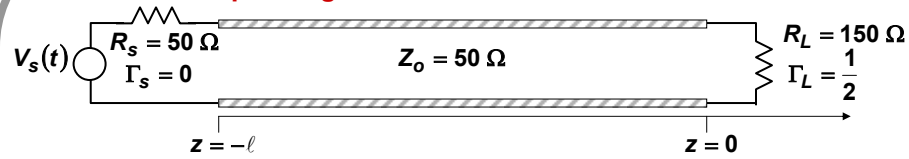Step Voltage Source: Turn-Off Transient - I




Suppose the source voltage has been at 4 Volts for a long time – but is shut off at time $t = 0$

$$V_s(t) = 4[1 - u(t)]$$

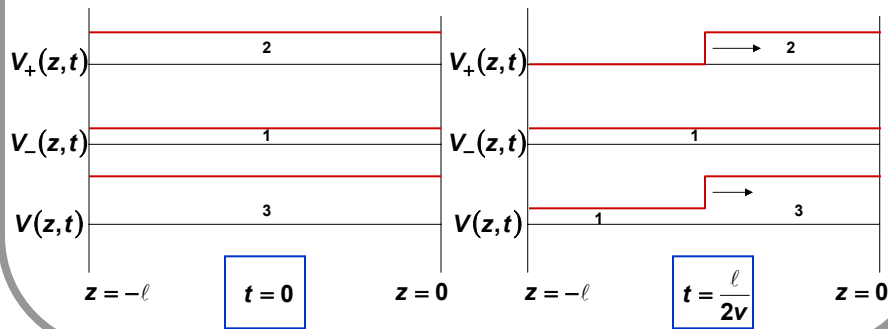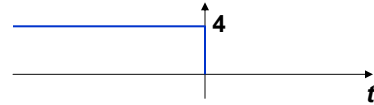


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

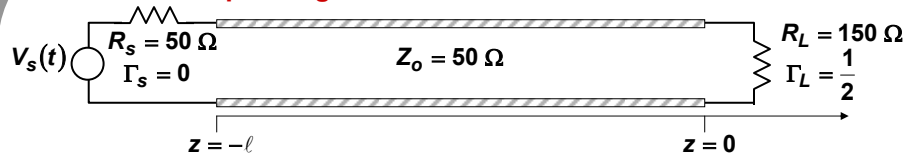Step Voltage Source: Turn-Off Transient - II




• After a time greater than $2\ell/v$ the line voltage is at constant 0 Volts

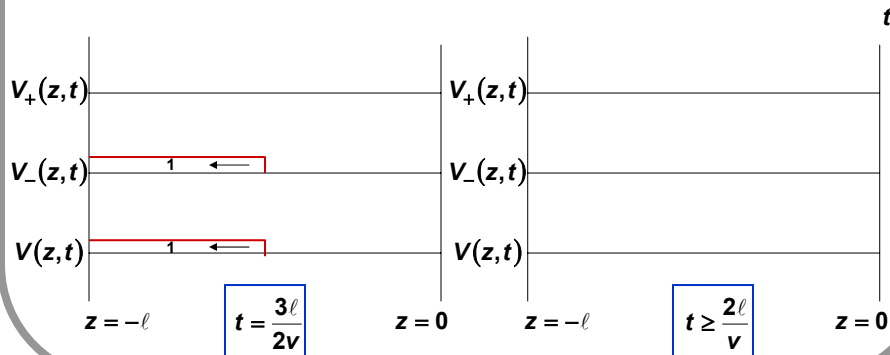


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Step Voltage Source: Turn-On Transient – General Case

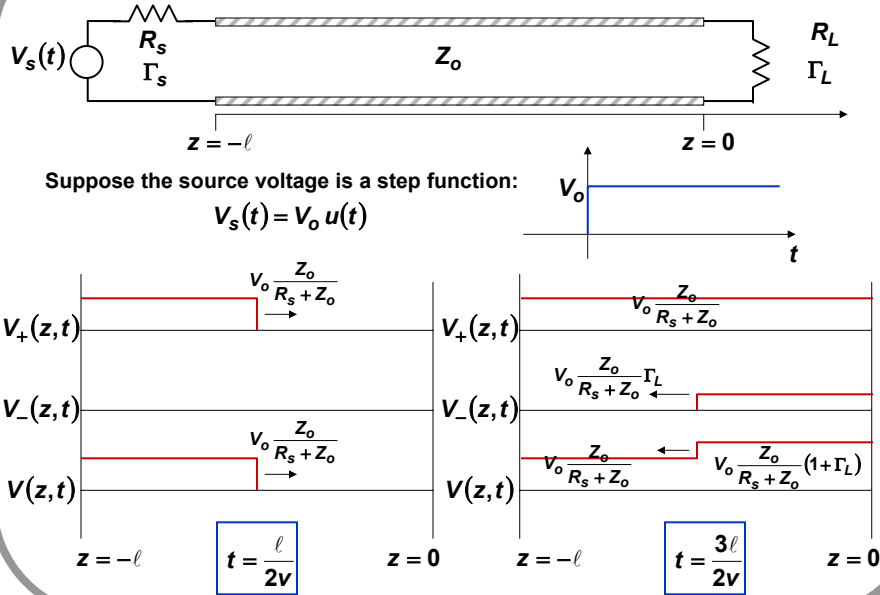


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Step Voltage Source: Turn-On Transient – General Case


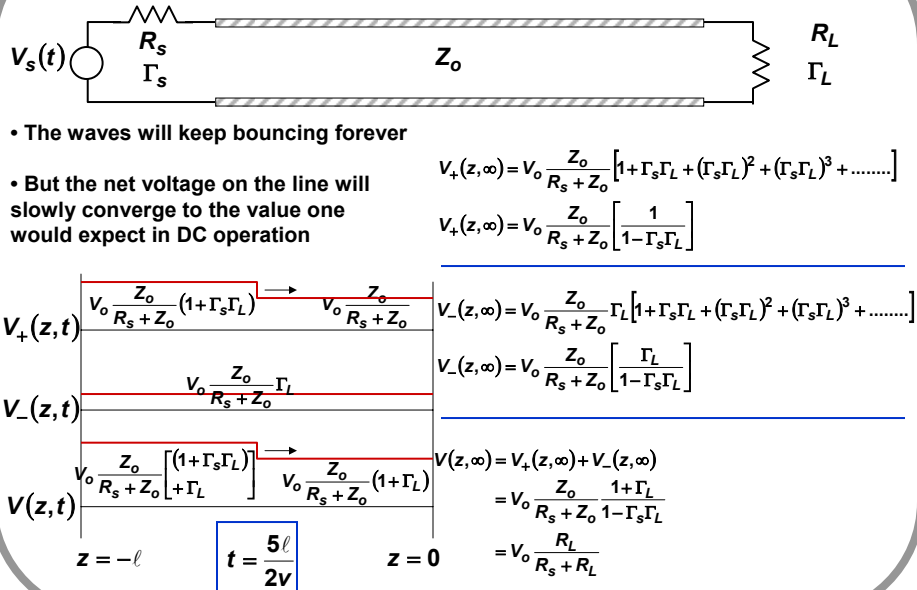


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Step Voltage Source: Turn-On Transient

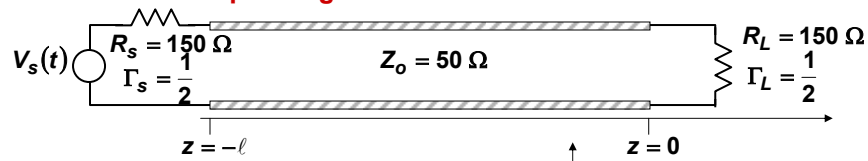


Source voltage is a step function: $V_s(t) = 1u(t)$

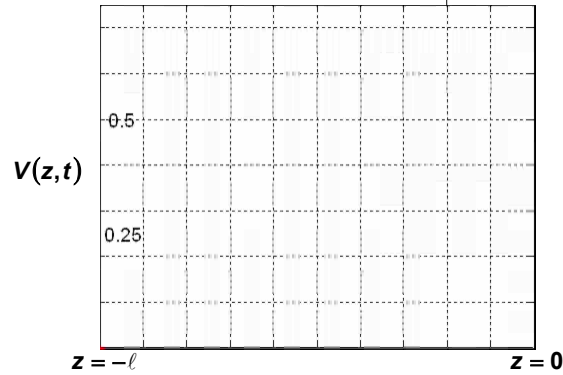
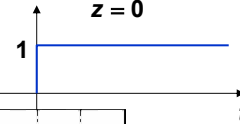


ECE 303 - Fall 2007 - Farhan Rana - Cornell University

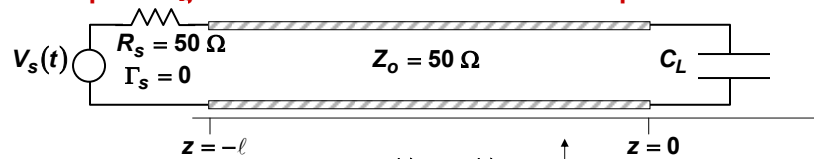Step Voltage Source: Turn-On Transient - Capacitive Load - I



Source voltage is a step function: $V_s(t) = 1u(t)$

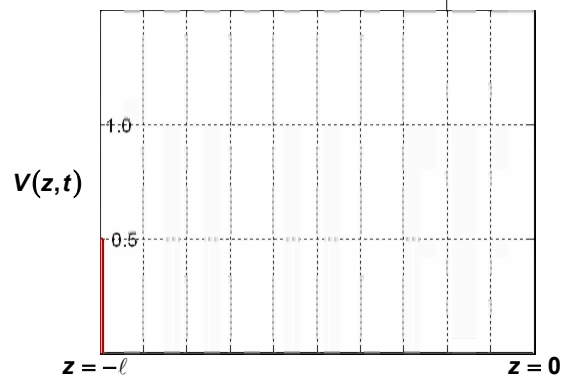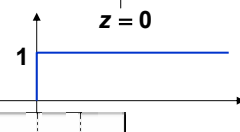


ECE 303 - Fall 2007 - Farhan Rana - Cornell University

Step Voltage Source: Turn-On Transient in a RC Circuit



Source voltage is a step function:


$$V_s(t) = 1u(t)$$

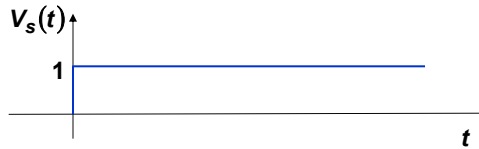

Solution for $V_C(t)$ is:


At short times the capacitor acts like a short
At long times the capacitor acts like an open

$$V_C(t) = \left(1 - e^{-\frac{t}{\tau}} \right) u(t)$$

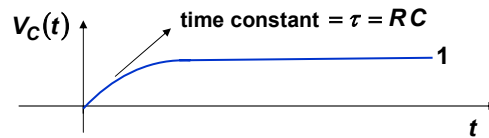


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

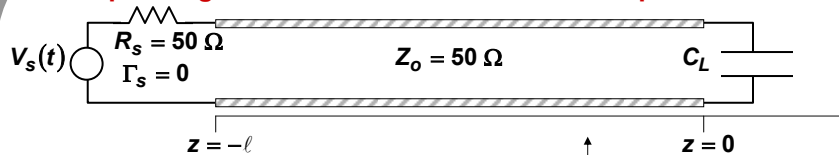Step Voltage Source: Turn-On Transient – Capacitive Load - II



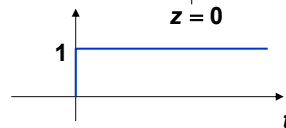
Source voltage is a step function: $V_s(t) = 1u(t)$



How does one solve this problem?

Transmission line is a linear system

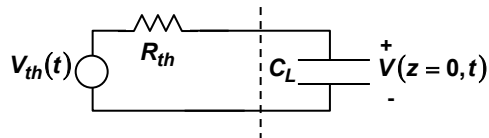So make a **Thevenin equivalent** circuit looking in from the load end



$$R_{th} = Z_0$$




This holds even if the source impedance were not matched to the line impedance (no such thing as impedance transformations in time domain)
This is because in transients situations it does not really matter what is on the other side of the line

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Step Voltage Source: Turn-On Transient – Capacitive Load - II

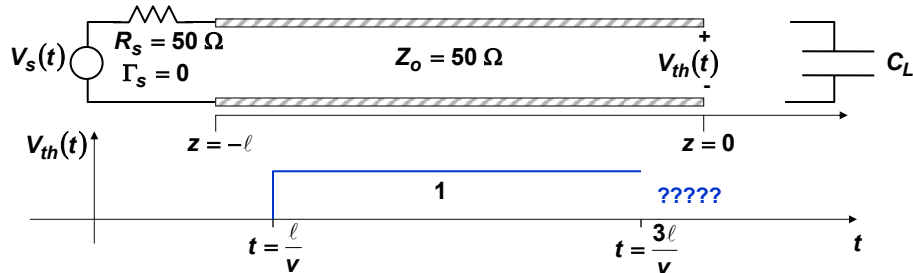
To find $V_{th}(t)$ remove the load capacitor and look at the open circuit voltage:



A forward voltage wave of 0.5 Volts from the source will reach the load at time $t = \frac{\ell}{v}$

A reflected voltage wave of 0.5 Volts will be generated at the same time $t = \frac{\ell}{v}$

$$\Rightarrow V_{th}(t) = 1 \quad \text{for} \quad \frac{\ell}{v} \leq t \leq \frac{3\ell}{v}$$


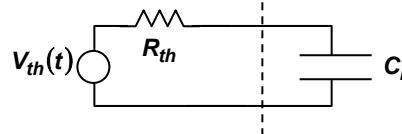


ECE 303 – Fall 2007 – Farhan Rana – Cornell University


Step Voltage Source: Turn-On Transient – Capacitive Load - III

So the Thevenin circuit for times $\frac{\ell}{v} \leq t \leq \frac{3\ell}{v}$ is:

$$R_{th} = Z_o$$

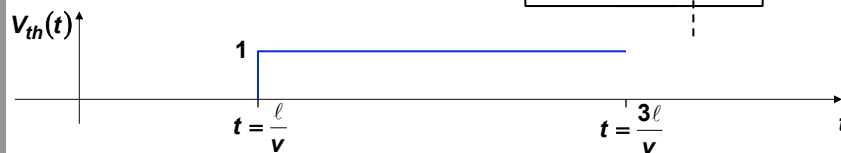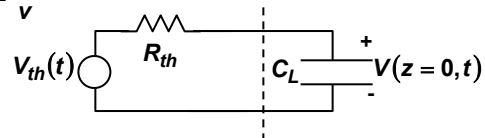


Solution for $V(z=0, t)$ is:

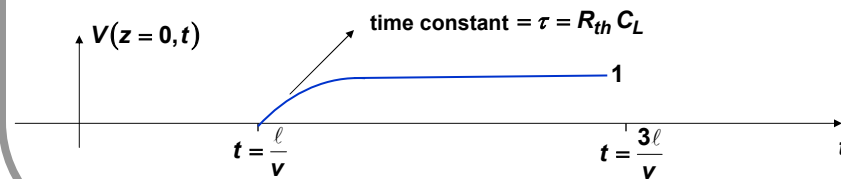


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Step Voltage Source: Turn-On Transient – Capacitive Load - IV

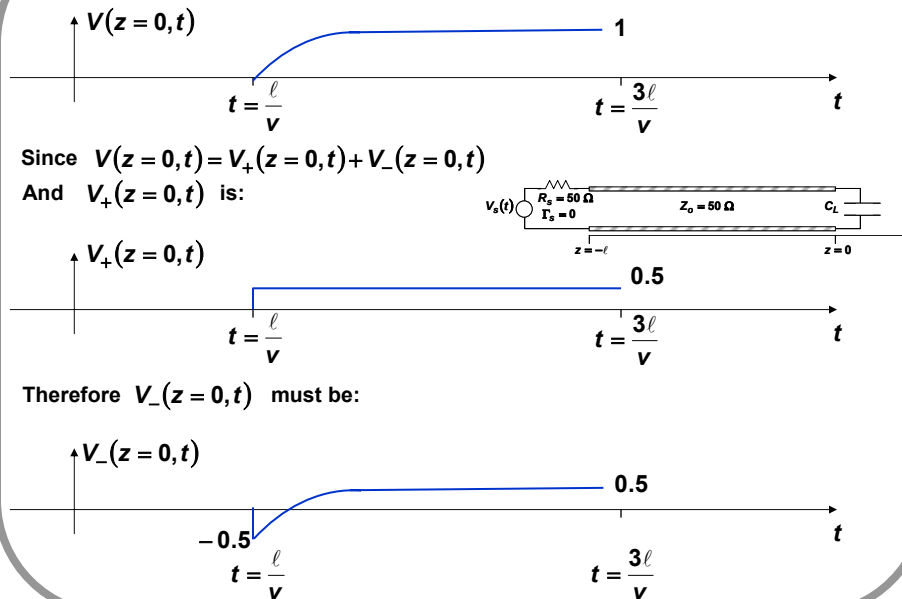


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Step Voltage Source: Turn-On Transient – Capacitive Load - V

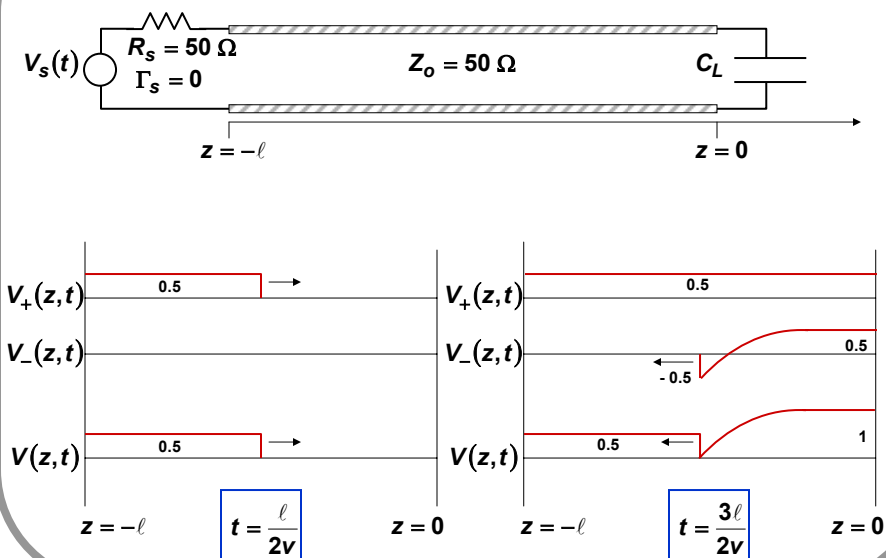


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Step Voltage Source: Turn-On Transient – Capacitive Load - VI

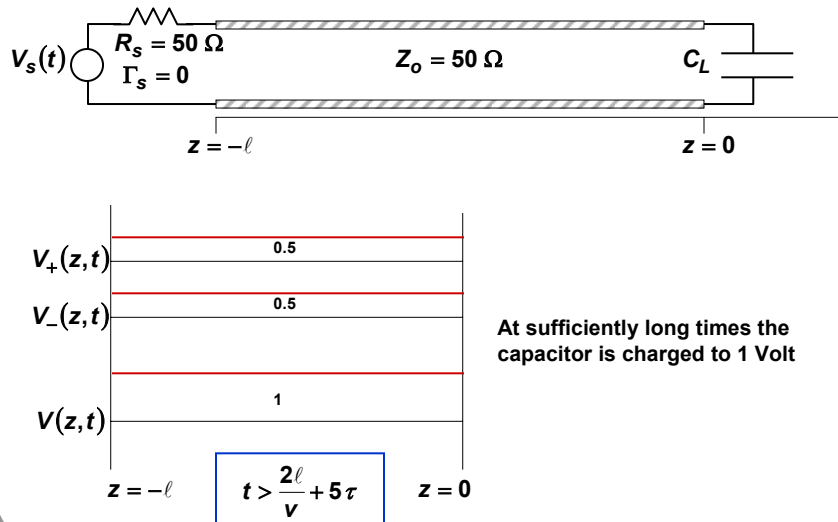


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Step Voltage Source: Turn-On Transient – Another Perspective

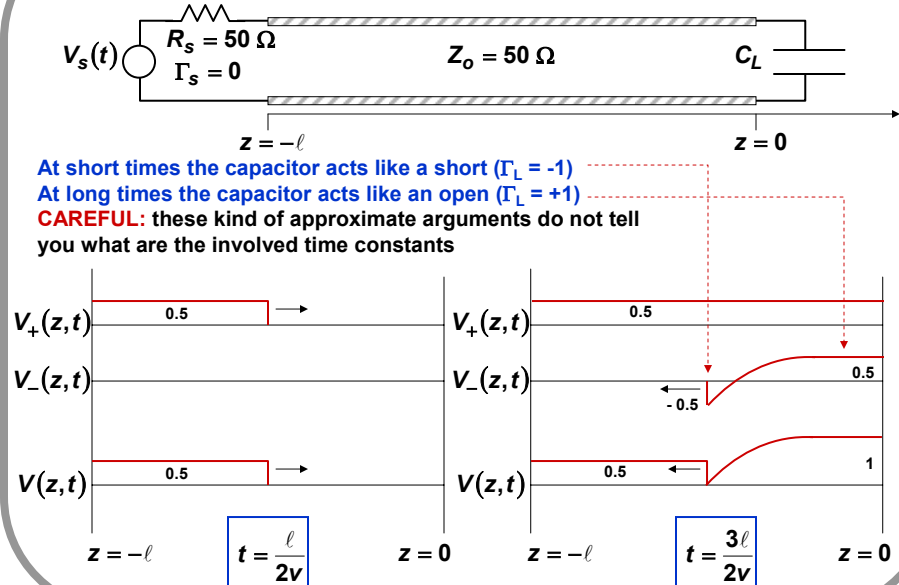


ECE 303 – Fall 2007 – Farhan Rana – Cornell University

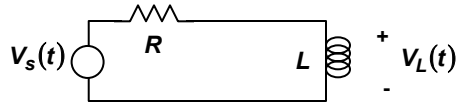Step Voltage Source: Turn-On Transient in a LR Circuit




Source voltage is a step function:

$$V_s(t) = 1u(t)$$

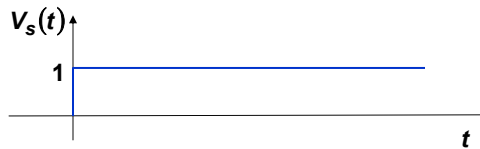


Solution for $V_L(t)$ is:

At short times the inductor acts like an open
At long times the inductor acts like a short

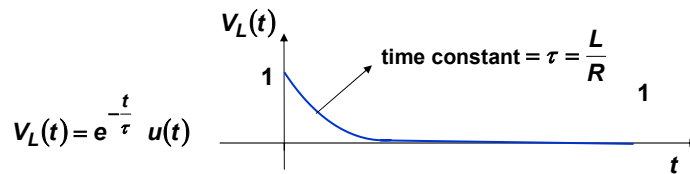

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

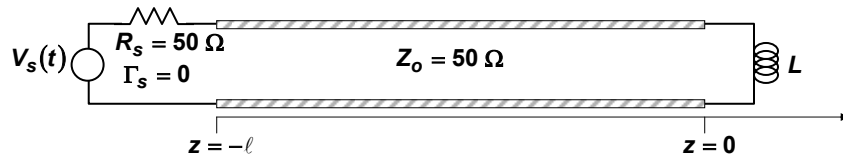
Step Voltage Source: Turn-On Transient –Inductive Load - I



Source voltage is a step function



At short times the inductor acts like an open ($\Gamma_L = +1$)

At long times the inductor acts like a short ($\Gamma_L = -1$)

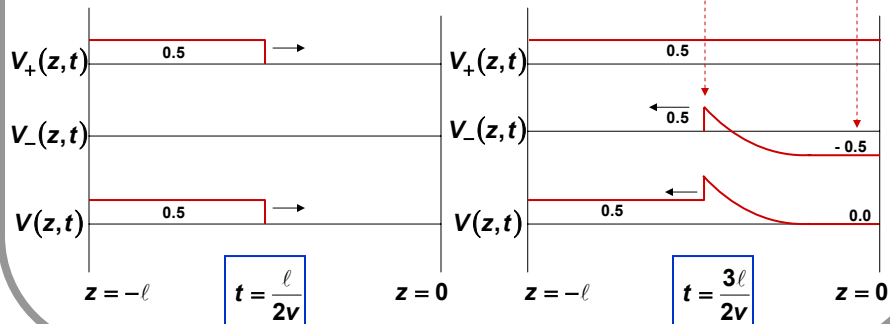

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

Step Voltage Source: Turn-On Transient – Inductive Load - II

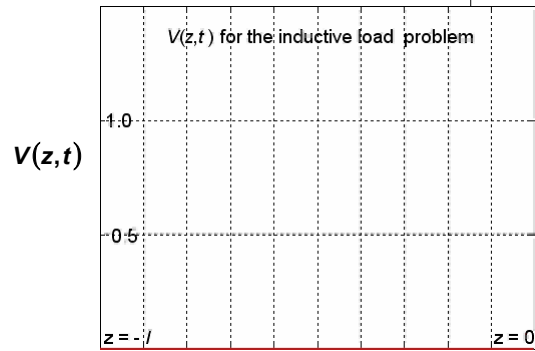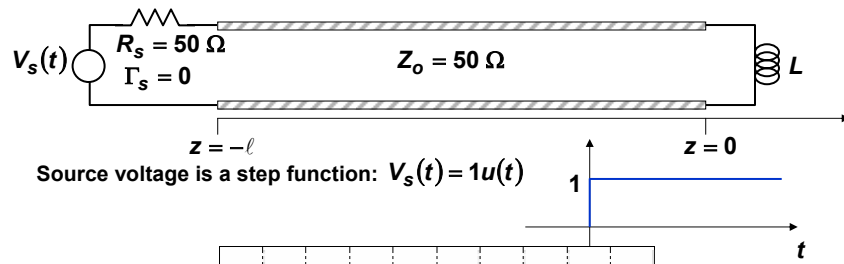

ECE 303 – Fall 2007 – Farhan Rana – Cornell University